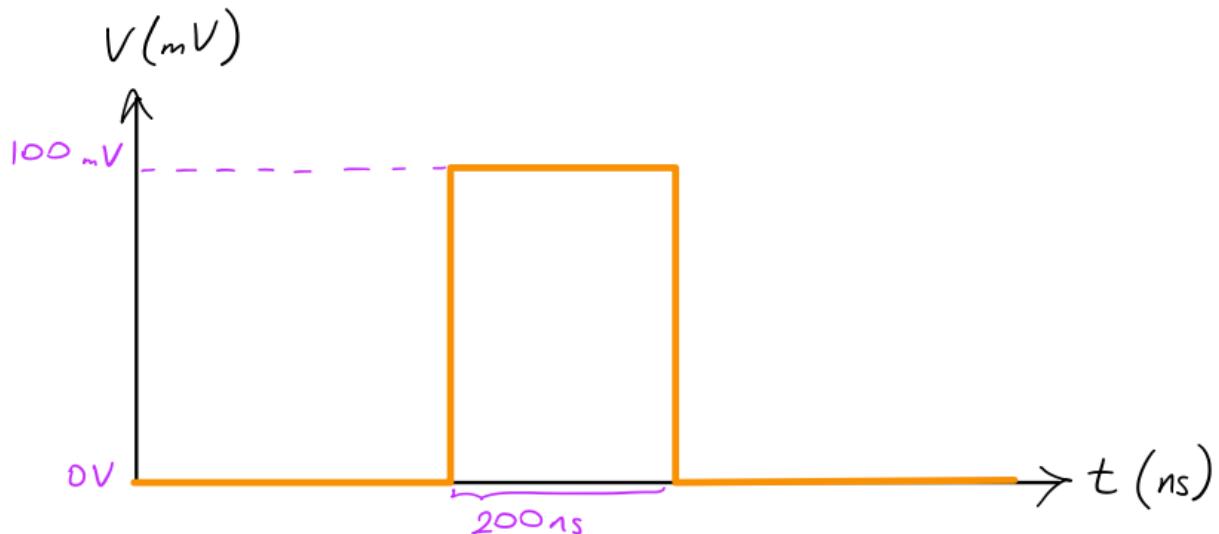


ECE320H1F: Fields and Waves
Laboratory 1: Waves On Transmission Lines

Deniz Uzun 1006035005 PRA0107

Marcos David Madrigal Albores 1004731347 PRA0108

- 3.2 [3] Sketch of the waveform at point C when the line is terminated in Z_0 .



- [2] Z_0 found using the variable load.

Z_0 is 50Ω .


- 3.3 [5] $Z_0 = v1(t, 0) / i1(t, 0)$ calculated using Ohm's law and measured voltages.

$$v1(t, 0) = 51.25 \text{ mV}$$


$$i1(t, 0) = 1 \text{ mA}$$

$$\begin{aligned} Z_0 &= v1(t, 0) / i1(t, 0) \\ &= (51.25 \text{ mV}) / 1 \text{ mA} \\ &= 51.25 \Omega. \end{aligned}$$

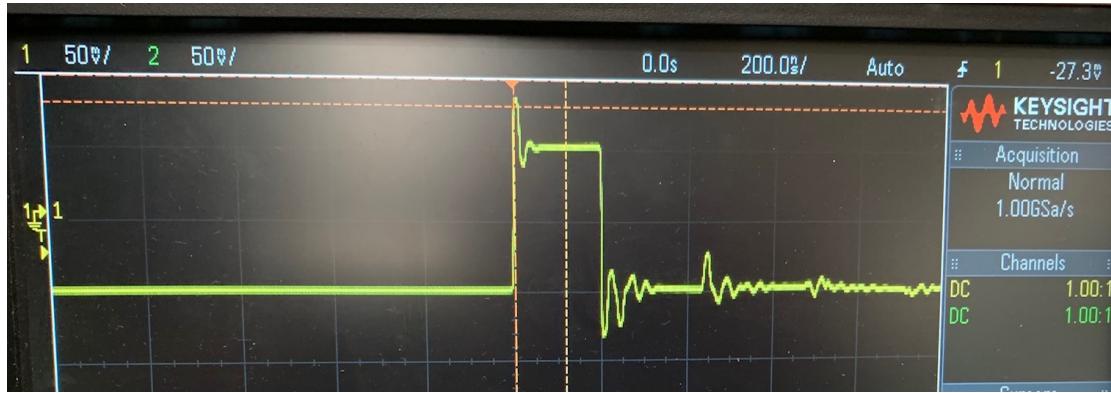3.4 [5] **Measurement** v vs t graphs at C, D, E, and F for $RL = 50 \Omega$.
At C at 0m



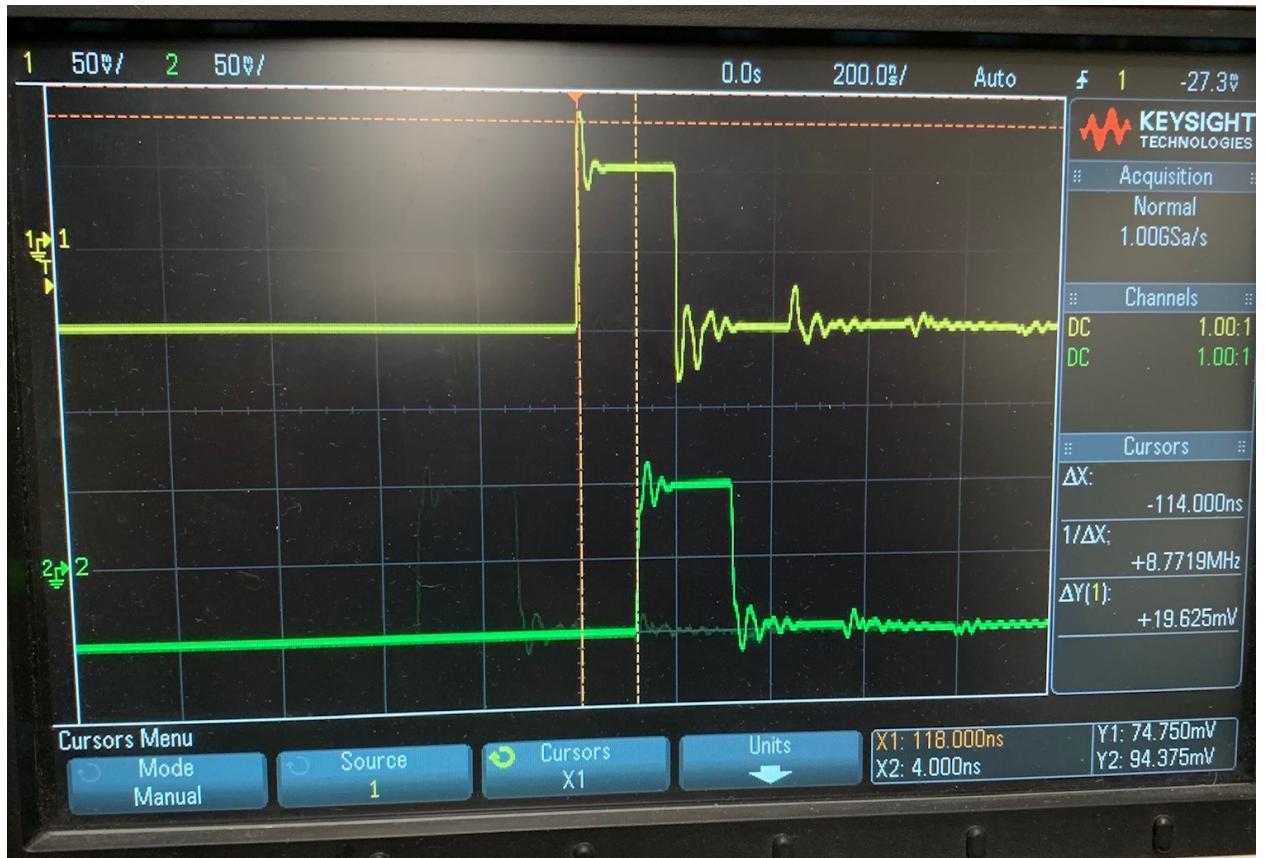At D at 30m (C on Channel 1 and D on Channel 2)



At E at 60m (C on Channel 1 and E on Channel 2)



At F at 90m (C on Channel 1 and F on Channel 2)



[3] Recorded time delay Δt at points D, E, and F relative to the input signal.

At D: 114 ns

At E: 232 ns

At F: 354 ns


3.5 [2] Calculated average velocity of propagation v_{avg} and relative permittivity ϵ_r .

v_{avg} : 2.631×10^8 m/s


ϵ_r : 1.30017

[10] Theoretical bounce diagram (2 marks) and corresponding v vs t graphs at C, D, E, and F (2 marks each). Compare with Section 3.4 measurement results.


Bounce Diagram (The line is matched.)

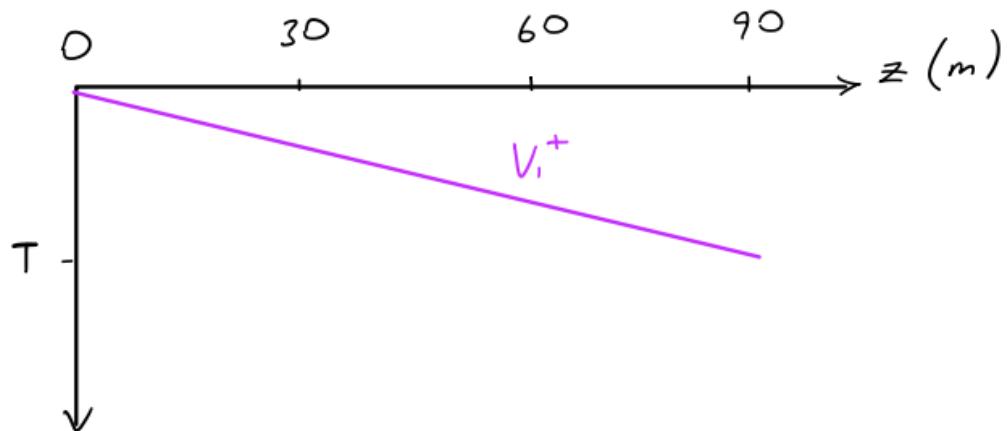


v vs t graph at C

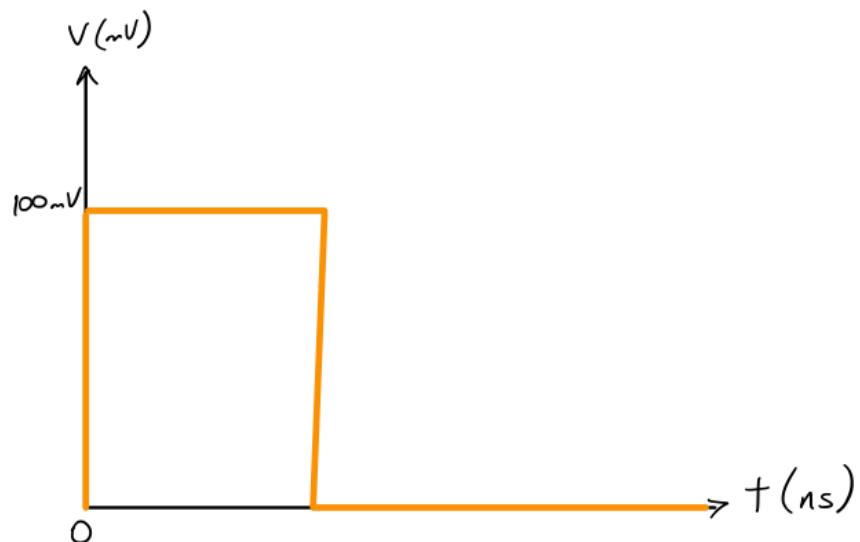


v vs t graph at D

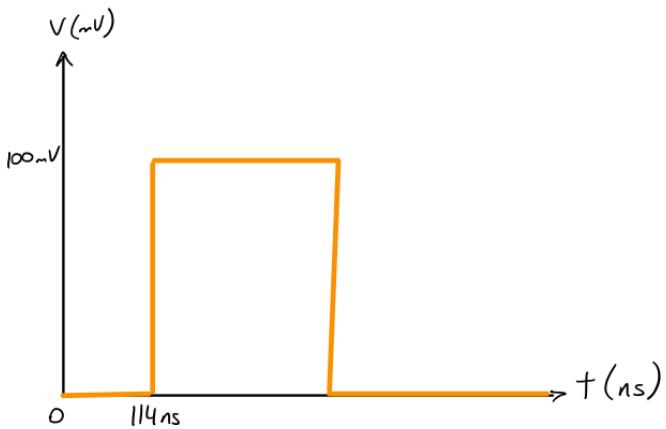

v vs t graph at E

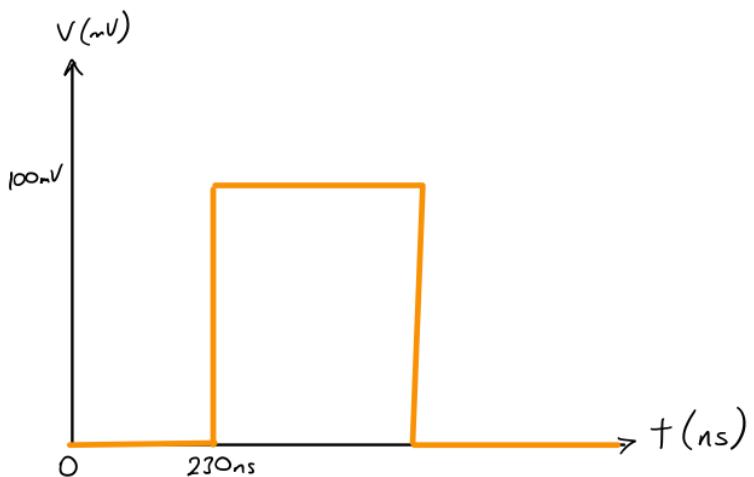

v vs t graph at F

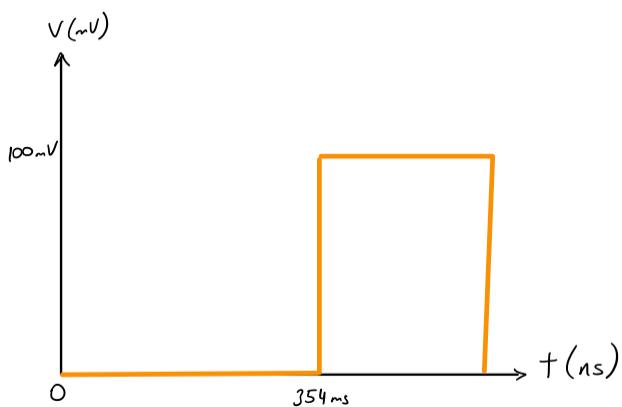

3.6 [1] Compare calculated and measured Γ_L .

Calculated Γ_L : 0.333

Measured Γ_L : 0.3

[4] Measurement v vs t graphs at C and F for $RL = 100 \Omega$.

Measurement at C and F (Channel 1 at C and Channel 2 at F)



[2] Discuss the relationship between the pulses at C and F.

From the graphs we can see that the pulse of F is delayed compared to C. This is because point F is at 90m on the transmission line so that it takes more time for the wave to receive that point. We can also observe that the pulses add up as they travel in opposite directions. Such process can be seen more clearly below:

Measurement at D vs C to observe reflective wave adding up on the initial wave




[10] Theoretical v vs d graphs at $t = T/2, T, 3T/2$, and $2T$ where $T = \text{pulsewidth}$.

$$36 \text{ J vs } d @ t = T/2, T, 3T/2 \text{ and } 2T \quad T \approx 7.94 \text{ ns}$$


$$Z_L = 100 \quad Z_0 = 50$$

$$T = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1}{3}$$

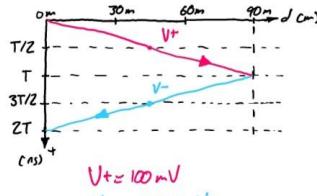
$$T_s = \frac{Z_L - Z_0}{Z_s + Z_0} = 0$$




(@) $T/2$

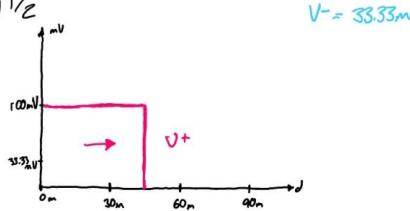


(@) T

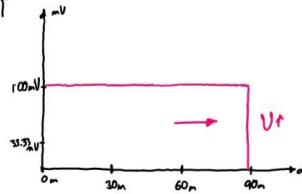

(@) $3T/2$

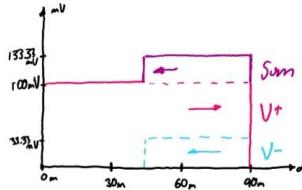

(@) $2T$

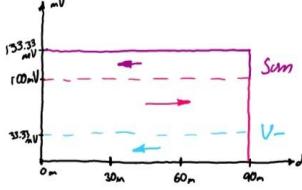

[2] Discuss the pulse propagation along the line with a mismatch at the load.

With a mismatch at the load we get reflections that bounce back and forth adding or subtracting from the initial wave until a convergence is reached.

3.7

[4] **Measurement** v vs t graphs at C and F for $R_{\text{source}} = (50 + 100) \Omega$ and $RL = 20 \Omega$ for pulse widths of T and $10T$.

Measurement at C on Channel 2 for pulse width T (Vg on Channel 1)



Measurement at F on Channel 2 for pulse width T (C on Channel 1)



Measurement at probably C and F for pulse width 10T (C on Channel 1 and F on Channel 2)



[2] Calculated and measured Γ_S and Γ_L .

$$\text{Calculated: } \Gamma_L = (Z_L - Z_0) / (Z_L + Z_0) = (20 - 50) / (20 + 50) = -3/7 = -0.4286$$

$$\Gamma_S = (Z_L - Z_S) / (Z_L + Z_S) = (20 - 150) / (20 + 150) = -13/17 = -0.7647$$

$$\text{Measured: } (1 + \Gamma_L) * V_o = 29.375 \text{ where } V_o = 50.625 \text{ V}$$

$$\Gamma_L = -0.419$$



$$V_o * \Gamma_L * \Gamma_S * (1 - \Gamma_L) = 9$$

$$(50.625) * (-0.419) * (\Gamma_S) * (1 - 0.419) = 9$$

$$\Gamma_S = 9 / [(50.625) * (-0.419) * (1 - 0.419)]$$

$$\Gamma_S = -0.7303$$

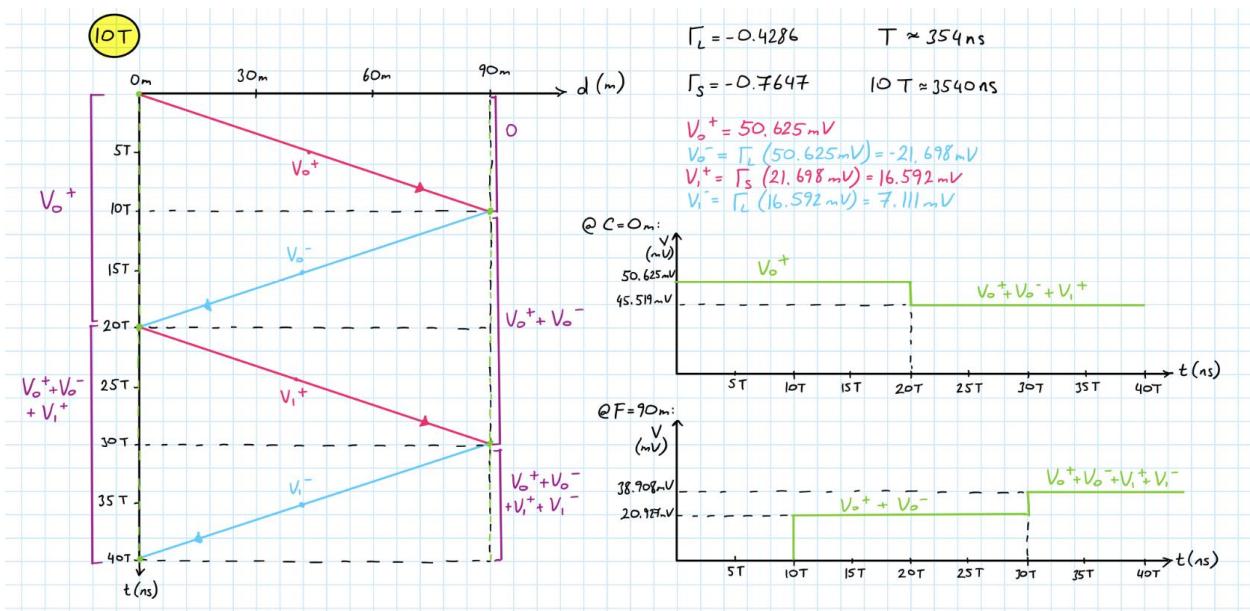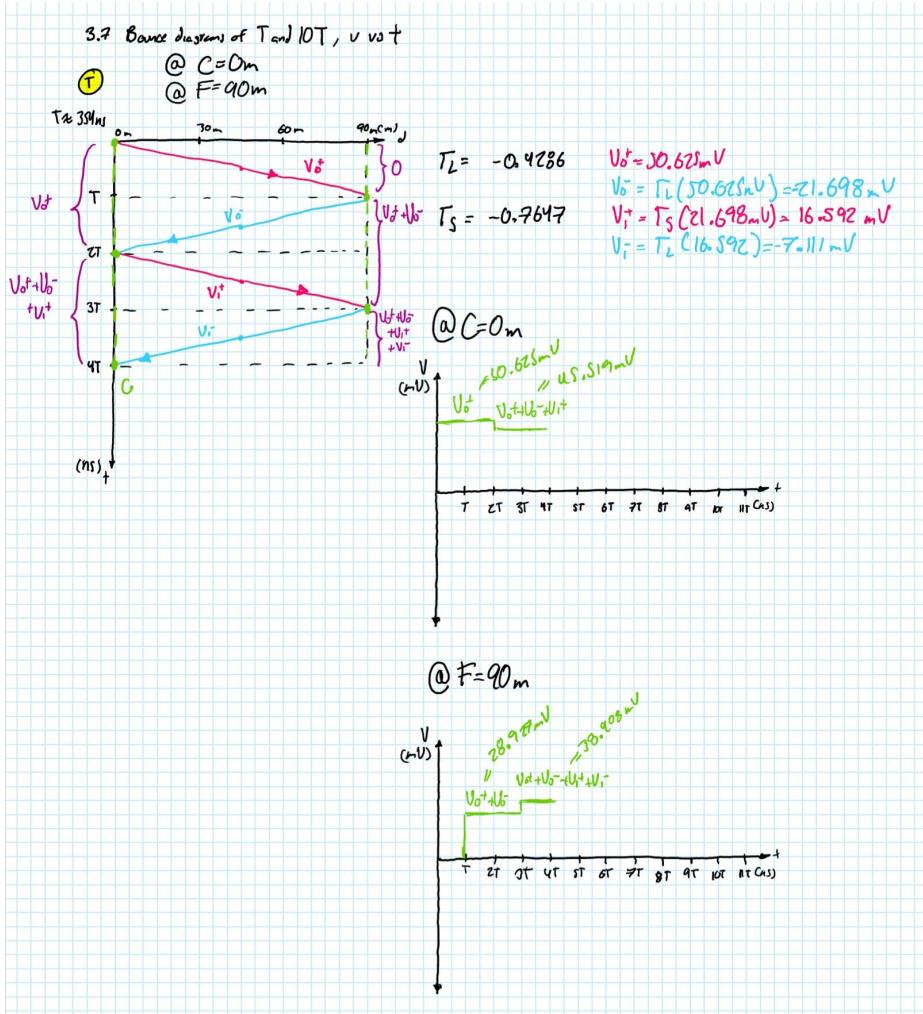[20] Calculate the corresponding theoretical bounce diagram diagram for pulse widths of T and $10T$ (5 marks each) and plot the theoretical v vs t graphs for each case at C and F (2.5 marks each).



[3] Discuss how the measured results compare to the theoretically calculated ones.

Measure results are almost equal to the calculated results. The small differences could be caused by estimations, device measurement accuracy and cursor placement.

3.8 [3] Find three v_1 minimum frequencies for the short circuit load.

1. 1.3MHz
2. 2.7MHz
3. 4.1MHz

[5] Explain why minimum voltages are obtained and discuss the effect on input current.

These minimum voltages are obtained at periodic intervals from the load due to the relationship between β and d (distance) and how they relate to λ at different frequencies, as these are the ones we are varying. When the load is short circuited the current is maximum and the voltage is minimum (the opposite can be argued for an open circuit equivalent where the current has minimum and voltage has a maximum).

[3] Find three v_1 minimum frequencies for the capacitive load.

1. 1.4MHz
2. 2.8MHz
3. 4.2MHz

[6] Discuss how and why the results for the short circuit and the capacitor are different.


For the short circuit load our frequency is 1.4MHz meaning that we get a minimum v_1 value every $T = 0.877 \mu s$. From the Smith Chart below, we can observe the outermost circle crosses the short circuit point (0,1) periodically as we loop around that circle.

For the capacitive load of capacitance $C = 0.01 \mu F$, our frequency is 1.4 as well, meaning that we get a minimum v_1 value every $T = 0.877$. As $Z_c = 1/j\omega C$ we can conclude that the normalized impedance (z_c) of the capacitive load will also have no real part and is purely reactive. Therefore it will also be on the same circle as the short circuit point which also has a real part of 0, in the Smith Chart. With this information we can conclude that the short circuit load and the capacitive load have repeated voltage minimas with the same span of time, as in the Smith Chart both are on the same circle with 0 resistance.

Although the frequency of occurrence is the same for both the short circuit and the capacitor case, we have different values for where the minimas occur. This is because the short circuit point and the capacitive load will be close but in different places in the Smith Chart, as they have different reactances. Therefore we can conclude that the frequencies would be similar but not the same.

The Complete Smith Chart

Black Magic Design

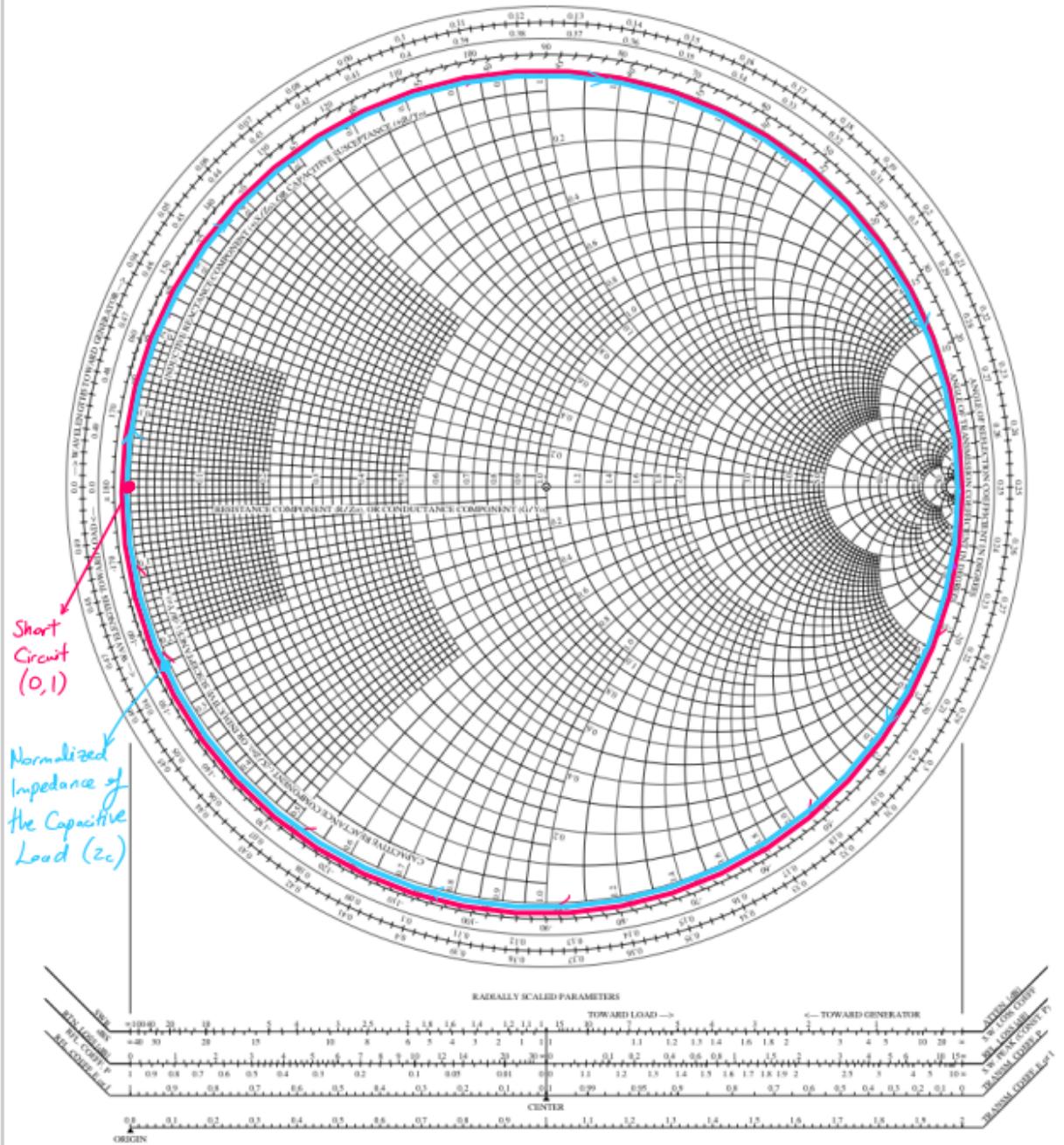

Capacitive Load $C = 0.01 \mu F$

$$\begin{aligned} Z_c &= \frac{1}{j\omega C} = \frac{1}{j^2 \pi f C} = \frac{1}{j^2 \pi 1.4 \cdot 10^6 \cdot 0.01 \cdot 10^{-6}} \\ &= \frac{1}{j 0.088} = \frac{-j}{0.088} = -11.368 j \Omega \end{aligned}$$

$$Z = \frac{Z_c}{Z_0} = \frac{-11.368 j}{50} = -0.227 j \Omega$$

Short Circuit $Z_{sc} = 0 + j0 \Omega$

[5] Presentation and neatness.

[] Indicates the number of marks out of 100 total marks